

## Electrical and Electro-Mechanical Systems

### Preliminaries

- Current ( $i$ ):

$$i = \frac{dQ}{dt} \text{ or } Q(t) = \int i \cdot dt$$

$i$ : current measured in Amperes 'A'  
 $Q$ : charge measured in Coulombs 'C'


- Voltage ( $v$ ): work per unit charge

$$v = iR \text{ } \} \text{ Ohm's law}$$

$$i = \frac{v_s}{R}$$

where  $v_s$  is the voltage source in measured in Volts 'V'

- Circuit Elements

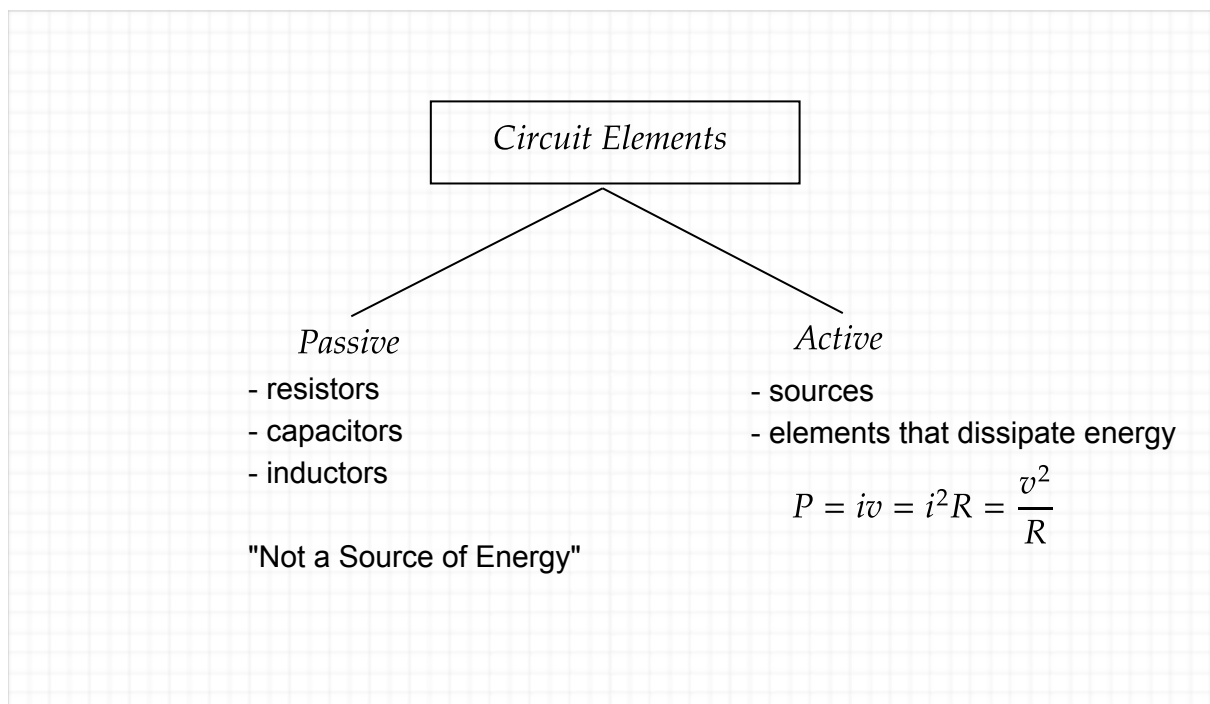

### Modeling Circuits

- Conservation of charge  $\Leftrightarrow$  Kirchoff's Current Law: Algebraic sum of the voltages around a closed loop or circuit must be zero.
- Sum of currents in a node = sum of currents out of a node
- Series Resistors  $\Rightarrow R_e = \sum_{i=1}^n R_i$
- Parallel Resistors  $\Rightarrow \frac{1}{R_e} = \sum_{i=1}^n \frac{1}{R_i}$

### Capacitance (C)

A capacitor is designed to store charge. (PUT SYMBOL)

Capacitance  $\Rightarrow C \Rightarrow$  measures of how much charge can be stored for a given voltage difference across the element:

$$v = \frac{1}{C} \int i \cdot dt = \frac{1}{C} \int_0^t i \cdot dt + \frac{Q_0}{C}$$

where  $Q_0$  is the initial charge in a capacitor at  $t = 0$ .

$$i = C \cdot \frac{dv}{dt}$$

### Inductance (L)

A magnetic field (a flu) surrounds a moving charge or current.

Inductor  $\Rightarrow L \Rightarrow$  (PUT SYMBOL) is a passive two-terminal electrical component that stores energy in a magnetic field when an electric current flows through it.

$$\phi = Li \Rightarrow \phi = \int v \cdot dt$$

$$i = \frac{1}{L} \int v \cdot dt$$

$$\therefore v = L \cdot \frac{di}{dt} \} \text{ where } L \text{ is measured in Henry (H)} \Rightarrow (v \cdot s / A)$$

## Power & Energy.

Power is stored/dissipated by an electrical element is:  $P = iv$

$$E \text{ in capacitor: } E = \int P \cdot dt = \int iv \cdot dt = \int \left( C \cdot \frac{dv}{dt} \right) v \cdot dt = c \int v dv = \frac{1}{2} C v^2$$

$$E \text{ in inductor: } E = \int P \cdot dt = \int iv \cdot dt = \int i \left( L \cdot \frac{di}{dt} \right) \cdot dt = L \int i di = \frac{1}{2} L i^2$$

$$P \text{ in resistor: } P = Ri^2 = \frac{v^2}{R}$$

## Electromechanical Systems

They are systems that have electrical and mechanical parts.

$$emf \implies v_b = K_b \omega \} \text{ voltage in armature}$$

$$T = K_T i_a \} \text{ torque in armature}$$

Usually the case is  $K_b = K_T$

where,  $v_b$  voltage in armature,  $K_b$  is motion backed emf &  $K_T$  motion torque